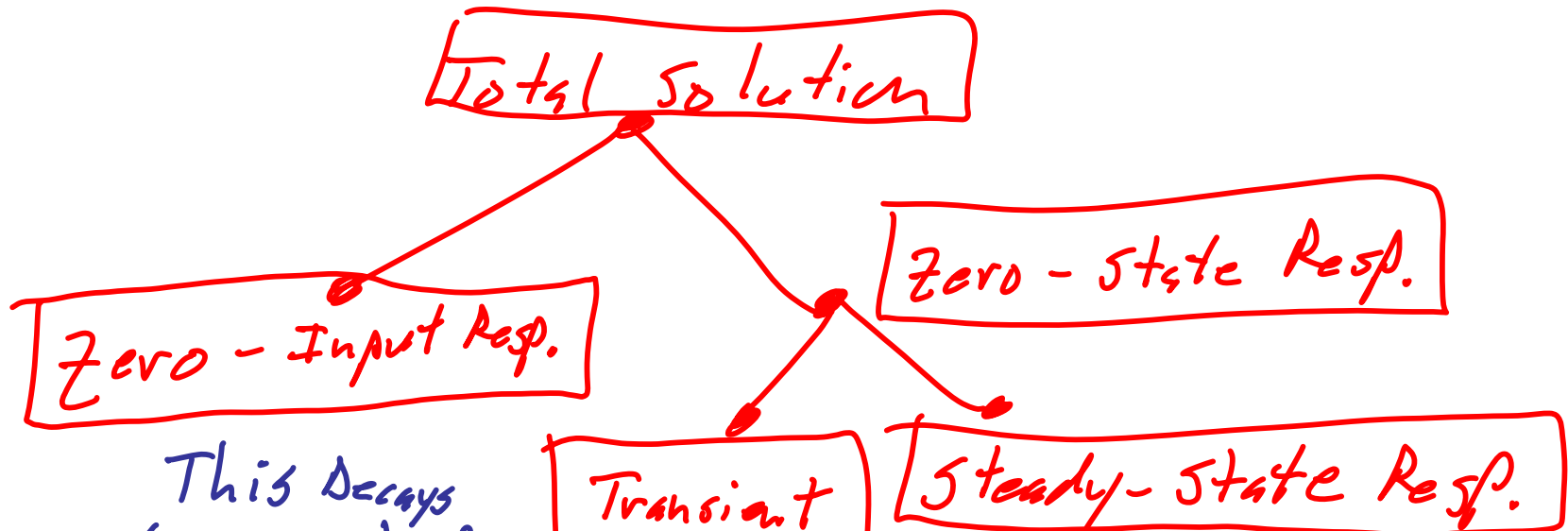


Example of LT Solution

(A)

First... A word about the 3 parts of the solution:



This Decays (transient) if the system is stable. Its behaviour is set by the

Transient Response

This Decays (transient) if the system is stable. Its behaviour is set by the

Steady-State Resp.


This might not decay. Its behaviour is set by the denominator of the Input $X(s)$

Den. of $H(s)$

→ Char. Poly & the PE's

→ Char. Poly

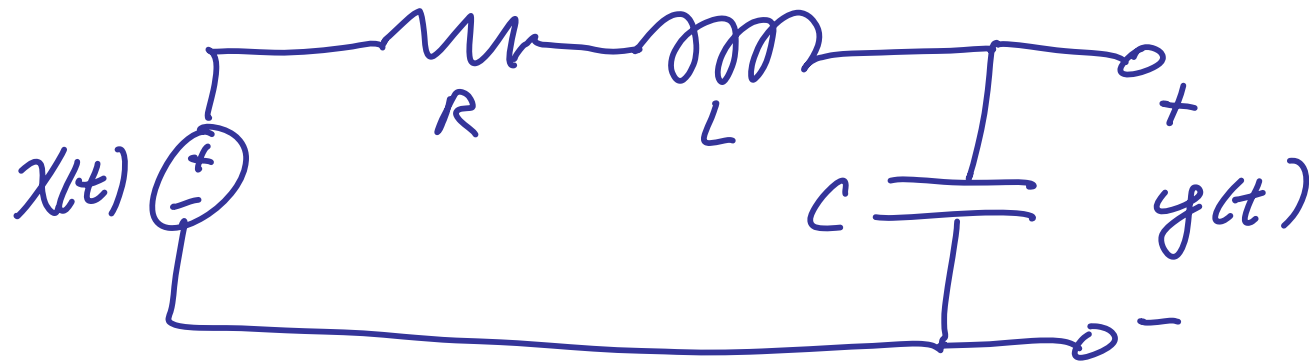For this problem consider the RLC series circuit (B)



We've seen that the Transfer Function is:

$$H(s) = \frac{1/LC}{s^2 + (R/L)s + 1/LC}$$

$$\text{Let } L = 100 \text{ mH} \quad C = 8.5 \mu\text{F} \quad R = 220 \Omega$$

$$\Rightarrow H(s) = \frac{B(s)}{A(s)} = \frac{1084.7^2}{s^2 + 2200s + 1084.7^2} = \frac{1084.7^2}{(s + 916.9)(s + 1283.1)}$$


(For this case we've seen that when $R > \frac{2L}{\sqrt{LC}}$ we get distinct real roots) ↗

The TF $H(s)$ captures the structure of the system and gives us everything we need to solve for the circuit's output! (c)

Suppose we have that:

ICs: $y(0^-) = 5$ $\dot{y}(0^-) = 2$

Input: $x(t) = 5 e^{-100t} u(t)$

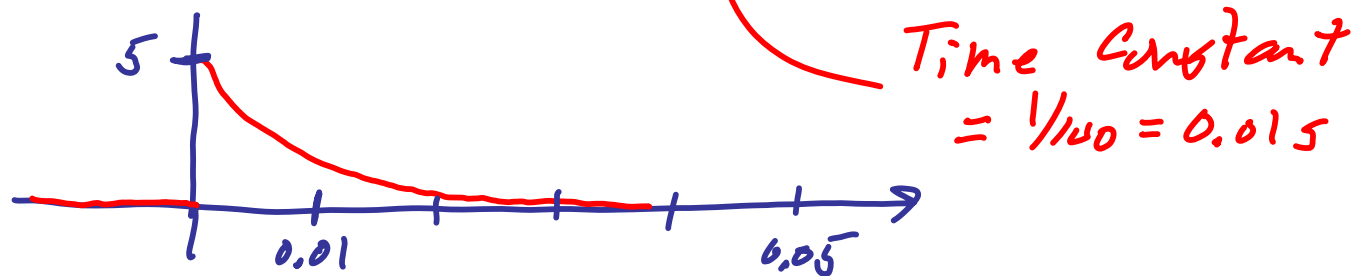

From LT table: $X(s) = \frac{5}{s+100}$

We have seen - "Note Set 33 - CT used to solve Diff Eq." - that a 2nd-order system has solution given by: (D)

$$Y(s) = \frac{y(0^-)s + [i(0^-) + a_1 y(0^-)]}{A(s)} + H(s) X(s)$$

zero-Input Part

zero-State Part

Now putting in for $A(s)$ & $H(s)$ gives:

$$Y(s) = \frac{y(0^-)s + [i(0^-) + 2200 y(0^-)]}{s^2 + 2200s + 1084.7^2} + \left[\frac{1084.7^2}{s^2 + 2200s + 1084.7^2} \right] X(s)$$

Note that $A(s)$ - the system's char. Poly. shows up here

Now plugging in the IC's gives:

$$Y(s) = \frac{5s + 11002}{s^2 + 22005 + 1084.7^2} + \left[\frac{1084.7^2}{s^2 + 22005 + 1084.7^2} \right] X(s)$$

Now plugging in X(s) gives:

$$Y(s) = \frac{5s + 11002}{s^2 + 22005 + 1084.7^2} + \left[\frac{1084.7^2}{s^2 + 22005 + 1084.7^2} \right] \left[\frac{5}{s + 100} \right]$$

$$= \frac{5s + 11002}{s^2 + 22005 + 1084.7^2} + \frac{5.9824 \times 10^6}{s^3 + 23005^2 + (1.3965 \times 10^6)s + (1.1765 \times 10^8)}$$

zero-Input Part...
has system char. Poly.
A(s) in Denominator

zero-state Part...
has combo of A(s) &
den of X(s) in Denominator

Note: Can use "conv"
command to compute
this! Just believe me...
or prove it yourself!

```
>> A=[1 (R/L) 1/(L*C)];
>> format long
>> Den=conv(A,[1 100])
Den =
1.0e+008 *
0.00000001000000 0.00002300000000 0.01396470588235 1.17647058823529
```

Now repeat last result here:

Zero-Input

Zero-State

(F)

$$Y(s) = \frac{5s + 11002}{s^2 + 2200s + 1084.7^2} + \frac{5.8824 \times 10^6}{s^3 + 2300s^2 + (1.3965 \times 10^6)s + (1.1795 \times 10^8)}$$

Do PFE on This

Do PFE on This

```
>>A=[1 (R/L) 1/(L*C)];
>>[R,P,K]=residue([5 11002],A)
```

```
R =
-12.5237
 17.5237
```

```
P =
1.0e+003 *
-1.2831
-0.9169
```

```
>>A=[1 (R/L) 1/(L*C)];
>>Den=conv([1 100],A);
>>[R,P,K]=residue(5*(1/(L*C)),Den)
```

```
R =
13.5763
-19.6628
 6.0864
P =
1.0e+003 *
-1.2831
-0.9169
-0.1000
```

Same
These are roots of char. Poly. A(s)!!

root of $s+100$ - the Den. of $X(s)$!!

$$Y(s) = \left[\frac{-12.52}{s + 1283.1} + \frac{17.52}{s + 916.9} \right] + \left[\frac{13.58}{s + 1283.1} + \frac{-19.66}{s + 916.9} \right] + \frac{6.09}{s + 100}$$

$$Y(s) = \left[\frac{-12.52}{s+1283.1} + \frac{17.52}{s+916.9} \right] + \left[\frac{13.58}{s+1283.1} + \frac{-19.64}{s+916.9} \right] + \frac{6.09}{s+100}$$

Factors of Char. Poly A(s)

Factors of Char. Poly A(s)

Den. of X(s)

Zero-Input Part

Zero-state Part

General Rules!!

- Transient Due to Input - is the part of z.s Resp. that is due to the factors of A(s)
- Steady-State Resp to Input - is the part of z.s Resp. that is due to the factors of the Den. of X(s)

Now use the LT table to invert: (11)

$$Y(s) = \left[\frac{-12.52}{s+1283.1} + \frac{17.52}{s+916.9} \right] + \left[\frac{13.58}{s+1283.1} + \frac{-19.66}{s+916.9} \right] + \frac{6.09}{s+100}$$

$$y(t) = -12.52 e^{-1283.1t} u(t) + 17.52 e^{-916.9t} u(t) \leftarrow \text{ZI Part}$$
$$+ 13.58 e^{-1283.1t} u(t) - 19.66 e^{-916.9t} u(t) \leftarrow \text{ZS Trans. Part}$$
$$+ 6.09 e^{-100t} u(t) \leftarrow \text{ZS Steady State Part}$$

For this example the ZI part & ZS Trans. Part die out long before the Steady State Part decays away.